

**LAB #7: Series DC Circuits**


In this lab, the Series DC Circuit will be introduced. In a Series Circuit, only one current flows within the circuit, and the sum of all the voltages over each component will equal the voltage of the power supply (Kirchhoff's Voltage Law). Calculations and measurements of resistance, voltage, current, and power will be made to gain understanding about how the series circuit works. Show all calculations and use complete sentences when answering questions.

Equations:  $V_T = I * R_T$        $V_T = V_1 + V_2 + V_3 + \dots$        $R_T = R_1 + R_2 + R_3 + \dots$

$V_i = V_T * \frac{R_i}{R_T}$        $I = \frac{V_T}{R_T} = \frac{V_i}{R_i}$        $P_T = I * V_T$        $P_i = P_T * \frac{R_i}{R_T} = \frac{V_i^2}{R_i} = I^2 * R_i$

**PART I: Resistance In Series Circuits**

Given:

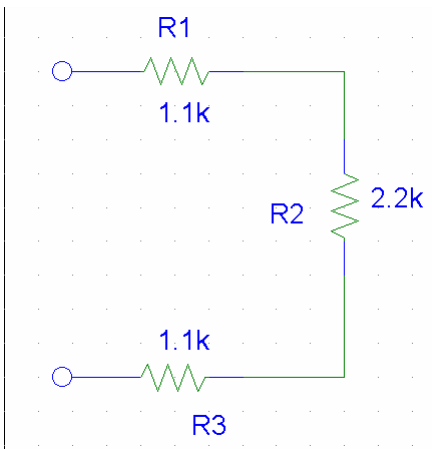

1. Calculate the Total Resistance ( $R_T$ ) of R1, R2 and R3.  
 (2 pts)

Calculated  $R_T =$  \_\_\_\_\_

2. Measure the resistance of each resistor using the Digital Multimeter and write them below. (2 pts ea.)

R1 = \_\_\_\_\_ R2 = \_\_\_\_\_ R3 = \_\_\_\_\_

3. Measure the Total Resistance ( $R_T$ ) of the circuit.  
 (2 pts)


Measured  $R_T =$  \_\_\_\_\_

4. What is the actual tolerance of the Total Resistance? (2 pts) \_\_\_\_\_

5. If it were desired to use **1** resistor instead of 3 to achieve the same  $R_T$ , what resistor could be used and why? (2 pts)

PART II: Voltage In Series Circuits

Given:

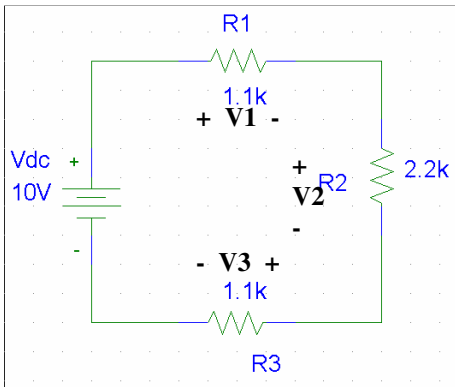

1. The Total Voltage ( $V_T$ ) of this circuit is equal to the voltage of the power supply. What is the Expected Total Voltage? (2 pts)

Expected  $V_T =$  \_\_\_\_\_

2. Measure the voltages V1, V2 and V3 (This is done by placing the leads of the ANALOG Multimeter over the corresponding resistor). BE SURE TO OBSERVE THE POLARITY. Write your measurements in the spaces provided. (2 pts ea.)

Measured: V1 = \_\_\_\_\_ V2 = \_\_\_\_\_ V3 = \_\_\_\_\_

3. What is the Total Voltage found by summing V1, V2, & V3? (2 pts)

$V_T = V1 + V2 + V3 =$  \_\_\_\_\_

4. Look at the measurements for V1 and V3. Write a sentence on the relationship of these voltages. (3 pts)

5. How do the resistances compare for the resistors corresponding to V1 and V3? (3 pts)


6. Now, look at the voltages V1 and V2. Write a sentence on what is observed about these voltages. (3 pts)

7. Again, what can be said about the resistances corresponding to V1 and V2. (3 pts)

8. What can be said about the voltage over a resistor ( $R_Y$ ) and the voltage over a resistor twice its value ( $R_X$ )? (3 pts)

PART III: Current In Series Circuits

Given:

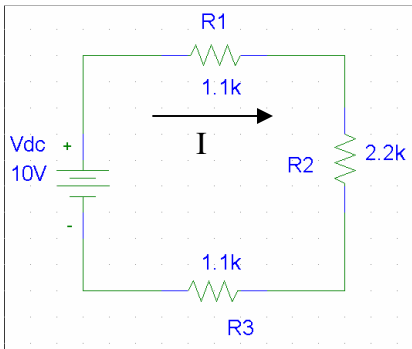

As can be seen in the circuit diagram there is only one current, I, that flows through the circuit.

This current can be found using various methods.

METHOD 1: FIND I USING  $V_T$  and  $R_T$

1. Calculate the Total Resistance ( $R_T$ ) (2 pts)

$R_T = \underline{\hspace{2cm}}$

2. What is the Total Voltage ( $V_T$ ) of the circuit? (2 pts)

$V_T = \underline{\hspace{2cm}}$

3. Calculate the Expected Current (I) of the circuit using  $V_T$  and  $R_T$ . (2 pts)

Calculated I =  $\underline{\hspace{2cm}}$

4. Measure the current through the circuit using the Digital multimeter. (2 pts)

Measured I =  $\underline{\hspace{2cm}}$

5. Does your measured value reflect your calculated value? (2 pts) (Y/N)  $\underline{\hspace{2cm}}$

METHOD 2: FIND I USING INDIVIDUAL VOLTAGE DROPS AND RESISTANCES

1. Calculate the current through each resistor. For V1, V2 and V3, use your measured values in PART II. (2 pts ea.)

$V_1 = I * R_1$

$V_2 = I * R_2$

$V_3 = I * R_3$

I =  $\underline{\hspace{2cm}}$


I =  $\underline{\hspace{2cm}}$

I =  $\underline{\hspace{2cm}}$

2. From the currents you calculated, what can you say about the current through the circuit? (3 pts)

PART IV: Determining the Power in Series Circuits

Given the following circuit:

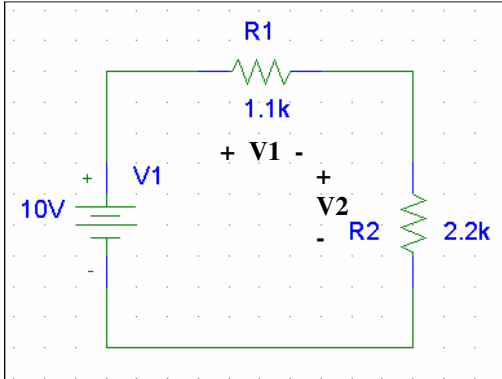

Initial Calculations: (2 pts ea.)

$R_T =$  \_\_\_\_\_

$I =$  \_\_\_\_\_

$V_1 =$  \_\_\_\_\_ (use  $R_1$  and  $I$ )

$V_2 =$  \_\_\_\_\_ (use  $R_2$  and  $I$ )

Power Calculations: (2 pts ea.)

Total Power:  $P_T =$  \_\_\_\_\_

The power of  $R_1$ :  $P_1 =$  \_\_\_\_\_ (Use the  $I$  and  $V_1$ )

The power of  $R_2$ :  $P_2 =$  \_\_\_\_\_ (Use the  $I$  and  $V_2$ )

Construct the circuit and take the following Measurements: (2 pts ea.)

$I =$  \_\_\_\_\_  $V_1 =$  \_\_\_\_\_  $V_2 =$  \_\_\_\_\_

$R_1 =$  \_\_\_\_\_  $R_2 =$  \_\_\_\_\_

From these measurements, calculate the following quantities: (2 pts ea.)

$P_T =$  \_\_\_\_\_  $P_1 =$  \_\_\_\_\_  $P_2 =$  \_\_\_\_\_

10. When adding  $P_1$  and  $P_2$ , is the result  $P_T$ ? (2 pts) (Y/N) \_\_\_\_\_

11. What does this say about the power of components in series and their relation to the total power? (3 pts)

