

### Laboratory Goals

- ❑ Familiarize students with the LM 555 IC and its uses
- ❑ Design a free-running oscillator
- ❑ Design a triggered one-shot circuit
- ❑ Compare actual to theoretical values for the circuits

### Pre-lab reading

- ❑ *Student Reference Manual for Electronic Instrumentation Laboratories* by Stanley Wolf and Richard Smith, Copyright 1990
- ❑ *National Semiconductor LM555 Data Sheet, found on the website*

### Equipment needed

- ❑ Lab notebook, pen
- ❑ Agilent E3631A Power Supply
- ❑ Agilent 34401A Digital Multimeter
- ❑ Agilent 54622 Digital Oscilloscope
- ❑ Agilent 33120A Function Generator
- ❑ 2 oscilloscope probes (attached to the oscilloscope)
- ❑ 1 test lead, BNC/EZ Hook
- ❑ 1 test lead, red, banana/EZ Hook
- ❑ 1 test lead, black, banana/EZ Hook

### Parts needed

- ❑ Circuit breadboard
- ❑ Lab parts kit
- ❑ IC, Timer/Oscillator, LM 555
- ❑ Capacitors, 2, ceramic disc, 0.01 $\mu$ F
- ❑ Capacitor, electrolytic, 68 $\mu$ F
- ❑ Resistors, 1K $\Omega$ , 180 $\Omega$ , 1/4 Watt
- ❑ Resistors, 3, (values to be determined), 1/4 Watt
- ❑ Red LED
- ❑ Jumper wires

### Lab safety concerns

- ❑ Make sure all circuit connections are correct, and no shorted wires exist.
- ❑ Adjust the power supply to the proper voltage before connecting it to the circuit
- ❑ Adjust signal generator to the proper level before connecting it to the circuit

**1. Pre-Lab LM 555 Designs**

Refer to the National Semiconductor LM555 Data Sheet, found on the website

- Design an astable multivibrator (free-running oscillator), referring to Figure 1 below. Choose the oscillation frequency to be the last 4 digits of your student ID number, and  $C$  to be  $.01 \mu\text{F}$ . Design the oscillator for a pulse width (PW) of  $.60$  (60%).

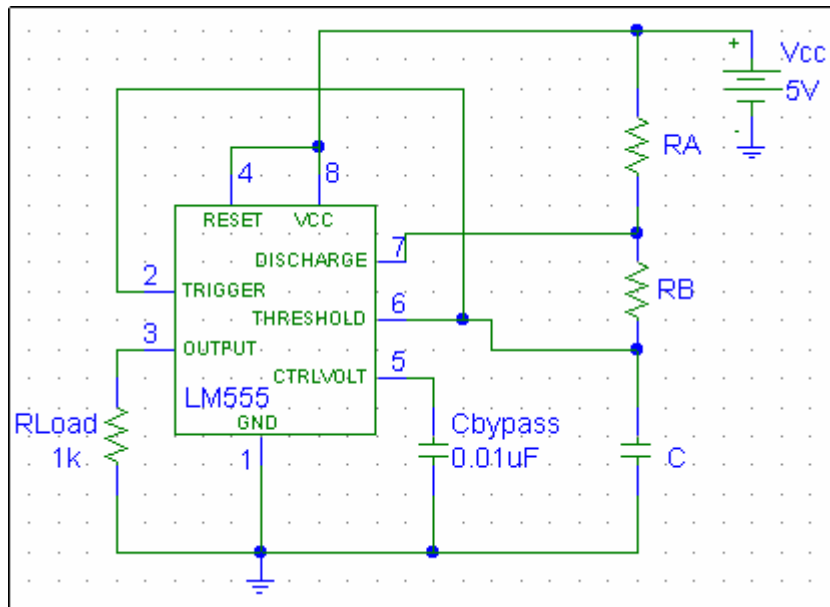


Figure 1 – LM555 Free-running Oscillator Schematic

- Design a monostable multivibrator (“one-shot”), referring to Figure 2 below. The hold time (i.e., the amount of time the circuit will hold its output in a high state) will be 1 second, and will light a Light-Emitting Diode (LED). Choose  $C$  to be  $68\mu\text{F}$ .
  - Calculate the current through  $R_d$ , which is the same as the current through the LED. Assume the LED to have a 1.5-volt drop, and the output of the 555 to be the same as  $V_{cc}$ .
  - We will use an electrolytic capacitor for  $C$ . Be careful to note the polarity. The negative terminal of the capacitor must be connected to the circuit ground. Electrolytic capacitors must be installed correctly or they may explode or leak.
  - The flat side of the LED (cathode) goes to circuit ground.

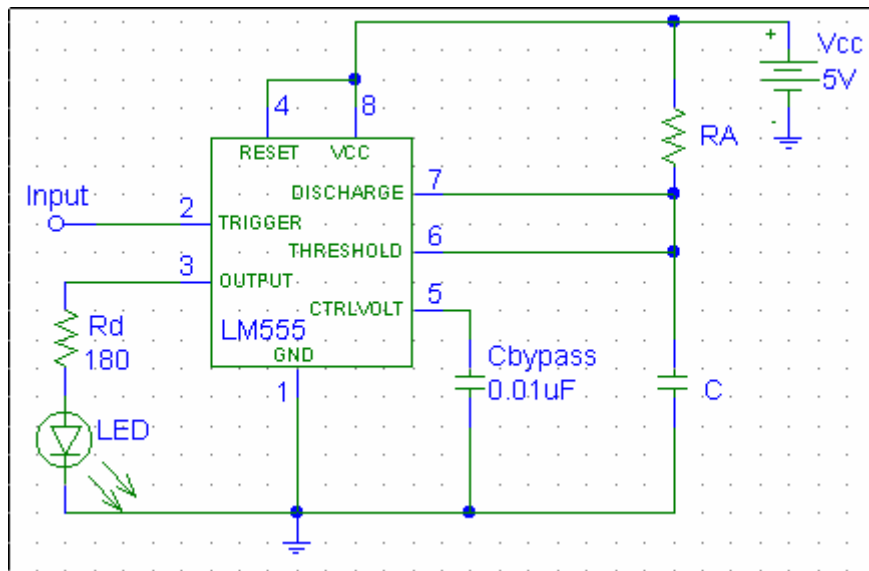


Figure 2 – LM555 “One-shot” Schematic


## 2. Circuit 1 Construction and Signal Measurement

- Before building the circuit, measure the values of all passive components (resistors and capacitors) and record the values in your lab notebook
- Build circuit 1 using the schematic (Figure 1), and your values of  $R_A$ ,  $R_B$ , and  $C$ . Resistors are probably not available in the calculated values: Use the nearest standard value found in the cabinet.

- ❑ Adjust the power supply to 5V, then connect it to the circuit Vcc and ground connections
- ❑ Connect the CH 1 oscilloscope probe and ground clip to the circuit output and circuit ground respectively
- ❑ Measure the output signal of the circuit. Record the pulse width, pulse period, frequency, amplitude, rise time, and overshoot in a table in your lab notebook
- ❑ Copy the output waveform to a diskette using the **Quick Print** option on the oscilloscope
  
- ❑ Disable the power supply output
- ❑ Disassemble the circuit
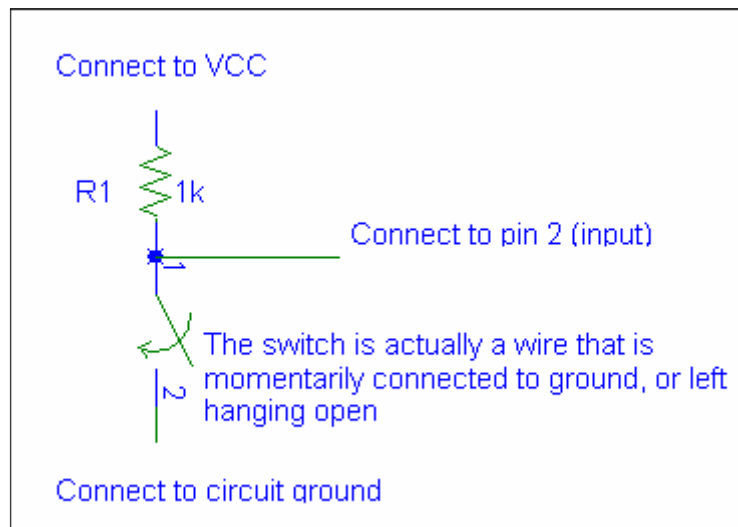
### 3. Circuit 2 Construction and Signal Measurement

- ❑ Build circuit 2 using the schematic (Figure 2), and your values of  $R_A$  and  $C$
- ❑ Attach the following input trigger circuit to pin 2:



- ❑ Connect the power supply to the circuit (still at 5VDC)
- ❑ Test the one-shot circuit by touching the wire to circuit ground several times within 1 second. (Notice that the LED remains lit for about 1 second, regardless of the number of times you touch the wire to circuit ground within 1 second)
- ❑ Disable the power supply output
- ❑ Disassemble the circuit

Before leaving the lab, take a few minutes to make sure all equipment and test leads are returned to your cabinet, and that you have cleaned up your work space.

#### **4. Analysis**

Write a summary report for this lab. Be sure to also include the following topics:

Compare theoretical vs. measured values, and calculate the percent error. Why might you see differences?

What applications can you think of to use these circuits?

Why is there a resistor in series with the Light Emitting Diode?

Explain any difficulties you had with this lab. (Please include suggestions to improve the lab, if you have them).